

Lab 1

Source Code

1. `cla_gl` source code

```
module cla_gl(
    output C3,          // carry output
    output[2:0] S,      // sum
    input[2:0] A, B,    // operands
    input C0            // carry input
);

// TODO:: Implement gate-level CLA
wire [2:0] g, p;
wire c1, c2;
// my naming is bad, sorry~~

// c1 = g0 | (p0 & c0)
OR xb0(p[0], A[0], B[0]);
AND ab0(g[0], A[0], B[0]);
AND pc0(cp0, p[0], C0);
OR c_1(c1, g[0], cp0);
FA fa0(tmpc0, S[0], A[0], B[0], C0);

// c2 = g1 | (g0 & p1) | (c0 & p0 & p1)
OR xb1(p[1], A[1], B[1]);
AND ab1(g[1], A[1], B[1]);
AND gp_1(gp1, g[0], p[1]);
AND4 cpp_1(cpp1, 1, C0, p[0], p[1]);
OR4 c_2(c2, g[1], gp1, cpp1, 0);
FA fa1(tmpc1, S[1], A[1], B[1], c1);

// c3 = g2 | (g1 & p2) | (g0 & p1 & p2) | (c0 & p0 & p1 & p2)
OR xb2(p[2], A[2], B[2]);
AND ab2(g[2], A[2], B[2]);
AND gp_2(gp2, g[1], p[2]);
AND4 gpp_2(gpp2, g[0], p[1], p[2], 1);
AND4 cppp_2(cppp2, C0, p[0], p[1], p[2]);
OR4 c_3(C3, g[2], gp2, gpp2, cppp2);
FA fa2(tmpc2, S[2], A[2], B[2], c2);
endmodule
```

2. `rca_gl` source code

```
module rca_gl(
    output C3,          // carry output
```

```


output[2:0] S,    // sum
input[2:0] A, B, // operands
input C0         // carry input
);
// TODO:: Implement gate-level RCA
wire C1, C2;
FA fa0(C1, S[0], A[0], B[0], C0);
FA fa1(C2, S[1], A[1], B[1], C1);
FA fa2(C3, S[2], A[2], B[2], C2);
endmodule

```

Waveform

Show the waveform of `cla_gl` on input transition from $000 + 000 + 0$ to $000 + 111 + 1$.

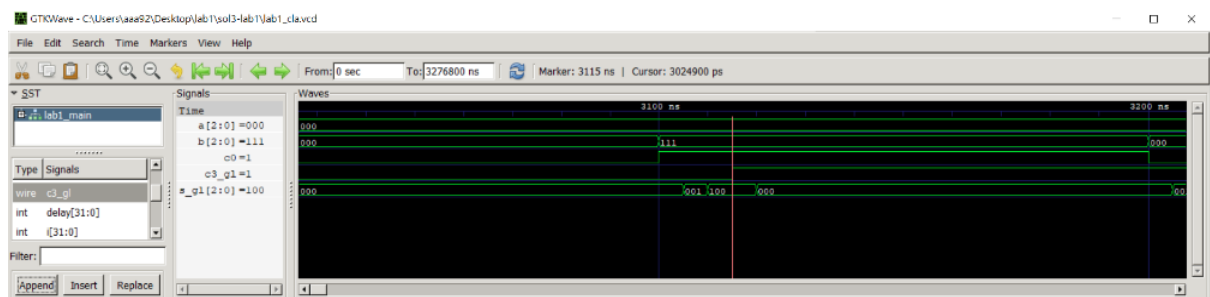You should select all the input and output signals of `cla_gl` module.



Propagation Delays

1. Find the maximum propagation delay of `rca_gl` and one of the corresponding input transitions.

23 ticks. From $000 + 000 + 0$ to $000 + 111 + 1$.

2. Find the maximum propagation delay of `cla_gl` and one of the corresponding input transitions.

20 ticks. From $000 + 000 + 0$ to $000 + 011 + 1$.

Some Derivation

Assume that only 2-input gates are used. Derive the number of levels needed in an n -bit carry-lookahead adder as a function of n .

C_n can be derived as follows.

$$\begin{aligned}
 C_1 &= G_0 + P_0 C_0 \\
 C_2 &= G_1 + G_0 P_1 + C_0 P_0 P_1 \\
 C_3 &= G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2 \\
 &\vdots \\
 C_n &= \sum_{i=0}^{n-1} \left(G_i \prod_{j=i+1}^{n-1} P_j \right) + C_0 \prod_{j=0}^{n-1} P_j
 \end{aligned}$$

The summation of $n + 1$ terms and the multiplication is of at most $n + 1$ terms, which implies $2 \lceil \log_2(n + 1) \rceil$ levels. Consider one level for P_i or G_i , # of level is $2 \lceil \log_2(n + 1) \rceil + 1$.

On the other hand, S_{n-1} is $C_{n-1} \oplus (A_{n-1} \oplus B_{n-1})$, which implies $2 \lceil \log_2 n \rceil + 2$ levels.

Combined, $\max\{2 \lceil \log_2(n + 1) \rceil + 1, 2 \lceil \log_2 n \rceil + 2\}$ is needed.